

More bits, circuits, adders (From the last class)

CS 2130: Computer Systems and Organization 1

Xinyao Yi Ph.D.
Assistant Professor

Announcements

- Quiz 2 out later today, due Sunday at 11:59pm
- Homework 1 due Monday
- Homework 2 available Monday

Adder

Can we use this in parallel to add multi-bit numbers?

What is missing?


Consider:

$$\begin{array}{r} 11 \\ +01 \\ \hline \end{array}$$


3-input Adder

Add 3 1-bit numbers: a , b , c


Ripple-Carry Adder

 


Ripple-Carry Adder: Lowest-order Bit

 

Ripple-Carry Adder: In General

 

Ripple-Carry Adder: In General

 


Clocks, Registers


CS 2130: Computer Systems and Organization 1

Xinyao Yi Ph.D.
Assistant Professor

What does this circuit do?

 


Increment Circuit

 


Gate Delay

What happens when I change my input?

 


Building a Counter

Building a Counter

 


Building a Counter - Waiting


1-bit Register Circuit

 

1-bit Register Circuit

 


1-bit Register Circuit

 


Building a Counter

Another Counter

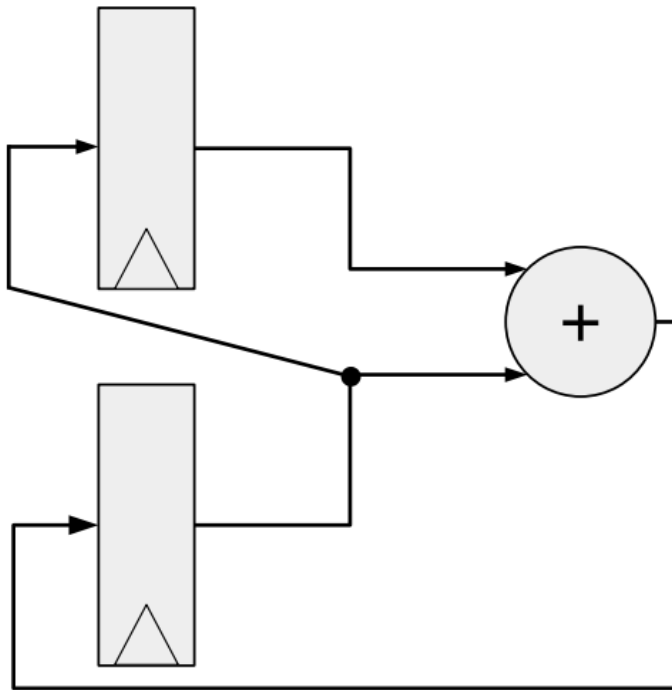

Another Counter

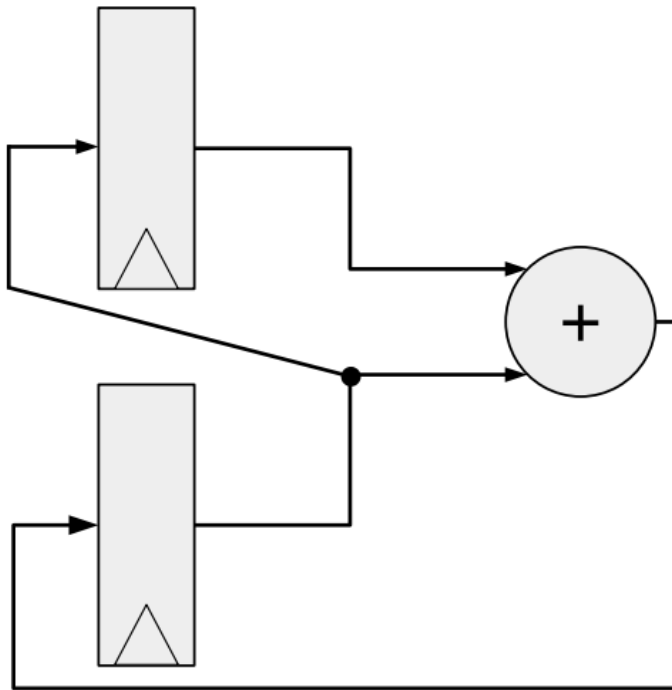

Common Model in Computers

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we already know: $\&$, $|$, \wedge , \sim
- Operations we can build from gates: $+$, $-$
- Others we can build:

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we already know: $\&$, $|$, \wedge , \sim
- Operations we can build from gates: $+$, $-$
- Others we can build:
- Ternary operator: $? :$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?

$x = 1$

$x = 0$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?
 $x = 1$
 $x = 0$
- **Single assignment:** each variable can only be assigned a value once

Any Questions?